

Study on the experimental behaviour of a linear resistor, capacitor, and inductor alternative-current circuit

Travaux pratiques génie électricité GIM 1 R1.04

Rong ZHOU Théo CUNY

11 décembre 2025

IUT Hubert Curien, Université de Lorraine, 7 Rue Fusillés Résistance, 88000 Épinal
ron@ronzz.org

Introduction

In this experiment, we aim to study the behaviour of a linear alternating-current circuit with components including resistors, capacitors, and inductors.

1 Part 1 : study of phase shift caused by a single electrical component

In this part, we connect our component of interest with a sinusoidal voltage source of a frequency of 100 Hz with an auxiliary resistor, as shown in Figure 1.

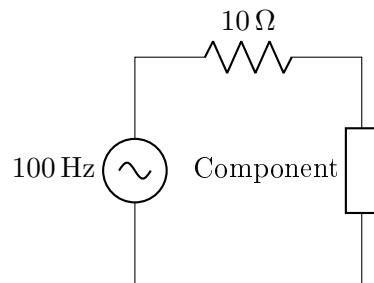


FIGURE 1 – Connection of the component with a sinusoidal voltage source and auxiliary resistor

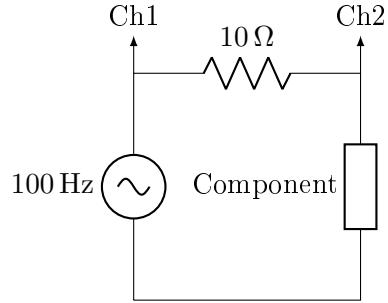


FIGURE 2 – Oscilloscope connection : Channel 1 to voltage source, Channel 2 to auxiliary resistor

Since a resistor causes zero phase shift, the phase shift between the voltage U and the current I of the circuit is equal to the phase shift between the source voltage U and voltage across the resistor U_R .

The oscilloscope measures temporal shift Δt , from which we can mathematically calculate the phase shift $\Delta\phi$ with the formula

$$\Delta\phi = \frac{2\pi \Delta t}{T},$$

where T is the period of the alternating voltage source.

1.1 1.1 : Study of phase shift caused by a single resistor

In this part, we use an auxiliary resistor of 10Ω and the tested resistor of 100Ω (Figure 3).

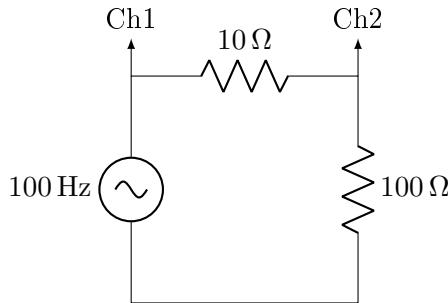


FIGURE 3 – Circuit with sinusoidal source, auxiliary resistor, and 100Ω resistor

We observed zero temporal shift for channel 1 with regard to channel 2, from which we deduce zero phase shift, in correspondence with theoretical expectations.

twidtthwidtth

FIGURE 4 – Oscilloscope output showing zero phase shift for the resistor circuit

1.2 1.2 : Study of phase shift caused by a single inductor

1.2.1 1.2.1 : Experimental determination

In this part, we use an auxiliary resistor of 100Ω with an inductor of 1 H (Figure 5).

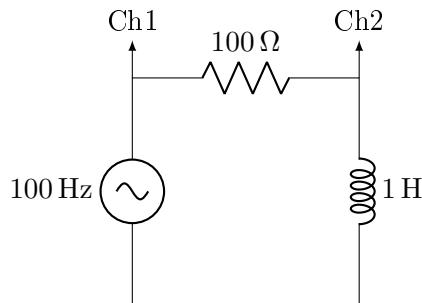


FIGURE 5 – Circuit with sinusoidal source, auxiliary resistor, and 1 H inductor

We observe a positive temporal shift of $\Delta t = 2.5\text{ ms}$ for channel 1 with regard to channel 2, from which we deduce a positive phase shift

$$\Delta\phi = \frac{2\pi \Delta t}{T} = \frac{\pi}{2},$$

in correspondence with theoretical expectations for an ideal inductor at that frequency.

twidtthwidtth

FIGURE 6 – Oscilloscope output showing positive phase shift for the inductor circuit

1.2.2 1.2.2 : Consideration of irrelevant variables

We are conscious that the resistance of the auxiliary resistor and the frequency of the alternating voltage source may impact our results. We have therefore varied them to study the effect.

With $f = 100\text{ Hz}$:

R_{aux} (Ω)	100	500	1000
Experimental temporal shift (ms)	2.25	1.5	1
Deduced phase shift	$\frac{\pi}{2}$	$\frac{3\pi}{10}$	$\frac{\pi}{5}$

As the value of R_{aux} increases, the measured phase shift reduces. From this we can conclude that an additional resistor in series will change the behaviour of the circuit. It is therefore in the interest of experimental precision to take a small R_{aux} .

With $R_{\text{aux}} = 1000\Omega$, varying frequency :

f (Hz)	100	75	10
Δt (ms)	2.25	3.75	10
Deduced phase shift	0.5π	0.56π	0.1π

As the value of f increases, the measured phase shift varies, which contradicts the simple theoretical expectation. We therefore conclude that frequency will impact the accuracy of our measurement. It is therefore preferable to take a reasonably large f , such as 100 Hz, for experimental precision.

1.3 1.3 : Study of phase shift caused by a single capacitor

1.3.1 1.3.1 : Experimental determination

In this part, we use an auxiliary resistor of 100Ω with a capacitor of $1\mu F$ (Figure 7).

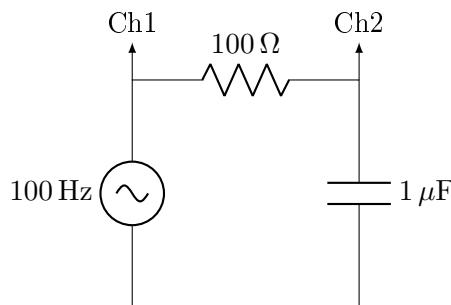


FIGURE 7 – Circuit with sinusoidal source, auxiliary resistor, and $1\mu F$ capacitor

We observe a negative phase shift for the capacitor. Experimentally, a temporal shift of $\Delta t = 1.5$ ms (sign depending on channel reference) corresponds to a phase shift magnitude of $\frac{3\pi}{10}$, in partial correspondence with theoretical expectations for an ideal capacitor at that frequency. The difference in experimental observation and theoretical expectations may be explained by experimental imprecisions and imperfections in equipments used, such as an important resistance in the circuit.

twidttwiddth

FIGURE 8 – Oscilloscope output showing negative phase shift for the capacitor circuit

1.3.2 1.3.2 : Consideration of irrelevant variables

Similar to section 1.2.2, we consider the irrelevant variables R_{aux} and f :

With $f = 100$ Hz :

R_{aux} (Ω)	100	500	1000
Experimental temporal shift (ms)	-2.5	-2.2	-1.6
Deduced phase shift	$-\frac{\pi}{2}$	-0.44π	-0.32π

As the value of R_{aux} increases, the measured phase shift magnitude reduces. It is therefore preferable to take a small R_{aux} for better precision.

With $R_{\text{aux}} = 1000 \Omega$, varying frequency :

f (Hz)	100	75	10
Δt (ms)	2.25	3.75	10
Deduced phase shift	0.5π	0.56π	0.1π

Again, frequency impacts the measured phase shift ; choose a sufficiently large and stable frequency for measurements (e.g. 100 Hz).

2 Part 2 : study of a RLC circuit in series under sinusoidal voltage

2.1 2.1 Experimental setup

In this part, we connect a sinusoidal voltage source of a frequency of 100 Hz with a resistor of 20Ω , an inductor of 0.2 H and a capacitor of $3 \mu\text{F}$ in series. Channel 1 of the oscilloscope is connected to the resistor, and channel 2 to the voltage source (Figure 9).

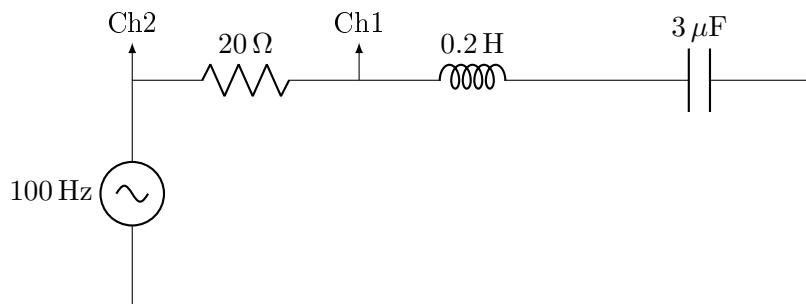


FIGURE 9 – Series RLC circuit with sinusoidal source, resistor, inductor, capacitor, and oscilloscope connections

2.2 2.2 Observations

Effective voltages From the oscilloscope we read effective voltages U of 21 V from the voltage source, and U_R of 7.39 V. The period is 10 ms, the frequency is 100 Hz, which translates into an angular frequency of $\omega = 2\pi f = 200\pi \text{ rad s}^{-1}$.

Phase shift We observe a positive temporal shift of channel 1 with regard to channel 2 of $\Delta t = 2.25 \text{ ms}$, from which we deduce a phase shift

$$\Delta\phi = \frac{2\pi \Delta t}{T} \approx 0.45\pi.$$

Figure 10 – Oscilloscope output for the series RLC circuit

Modeling If we model $U(t) = U_m \cos(\omega t)$, since $I_m = \frac{U_{Rm}}{R}$, so

$$I(t) = I_m \cos(\omega t - \frac{\pi}{2}) = I_m \sin(\omega t) = \frac{U_{Rm}}{R} \sin(\omega t).$$

From U_R , we use Ohm's law $I = \frac{U_R}{R}$ to calculate the effective current

$$I_{\text{eff}} = \frac{7.39}{20} = 0.3695 \text{ A} \approx 369.5 \text{ mA}.$$

Remarks With a phase shift $\Delta\phi \approx 0.45\pi$, this circuit behaves similarly to a predominantly inductive circuit, despite the presence of a resistor and a capacitor.

Conclusion

In this experiment, we were partially able to experimentally verify the phase shifts produced by an inductor and a capacitor in an AC circuit (approximately $+\frac{\pi}{2}$ and $-\frac{\pi}{2}$ respectively for ideal components). We also studied a series RLC circuit to observe the combined effect of multiple components; phase contributions combine and the resulting phase depends on the relative magnitudes of the impedances rather than a simple arithmetic sum.